

## **Laboratory Assignment #1**

**Due:** End of the lab section.

Follow the design steps below during the lab session:

- 1) Obtain the truth table and derive the corresponding K-map (*made as quiz*)
- 2) Obtain optimized Boolean expression from the K-map (*made as quiz*)
- 3) Draw the corresponding gate level circuit using any logical gates you want.
- 4) Enter your design using schematic editor in Xilinx ISE Design tool.
- 5) Simulate all possible input combinations in Xilinx ISE Design tool and make sure your design functions correctly in simulation. Check the correctness of your circuit using truth table.
- 6) For better visualization, group your inputs/outputs via “New Virtual Bus” option. Then, rename and change the radix of your virtual bus accordingly.
- 7) **Demonstrate your work to TA.**
- 8) Zip your project file and submit it to the SUCourse+.

Note that you must zip and submit your project directory (not just schematic file or testbench) to Lab#1 assignment. You must submit it until the end of your lab section (e.g. if your lab section is between 17:40-19:30, your deadline for submission is 19:30.).