

Registers & Counters

Logic and Digital System Design - CS 303


Sabanci University

Registers

- Registers are clocked sequential circuits
- A register is a group of flip-flops
 - Each flip-flop capable of storing one bit of information
 - An n-bit register
 - consists of n flip-flops
 - capable of storing n bits of information
 - besides flip-flops, a register usually contains combinational logic to perform some simple tasks
 - In summary
 - flip-flops to hold information
 - combinational logic to control the state transition

Counters



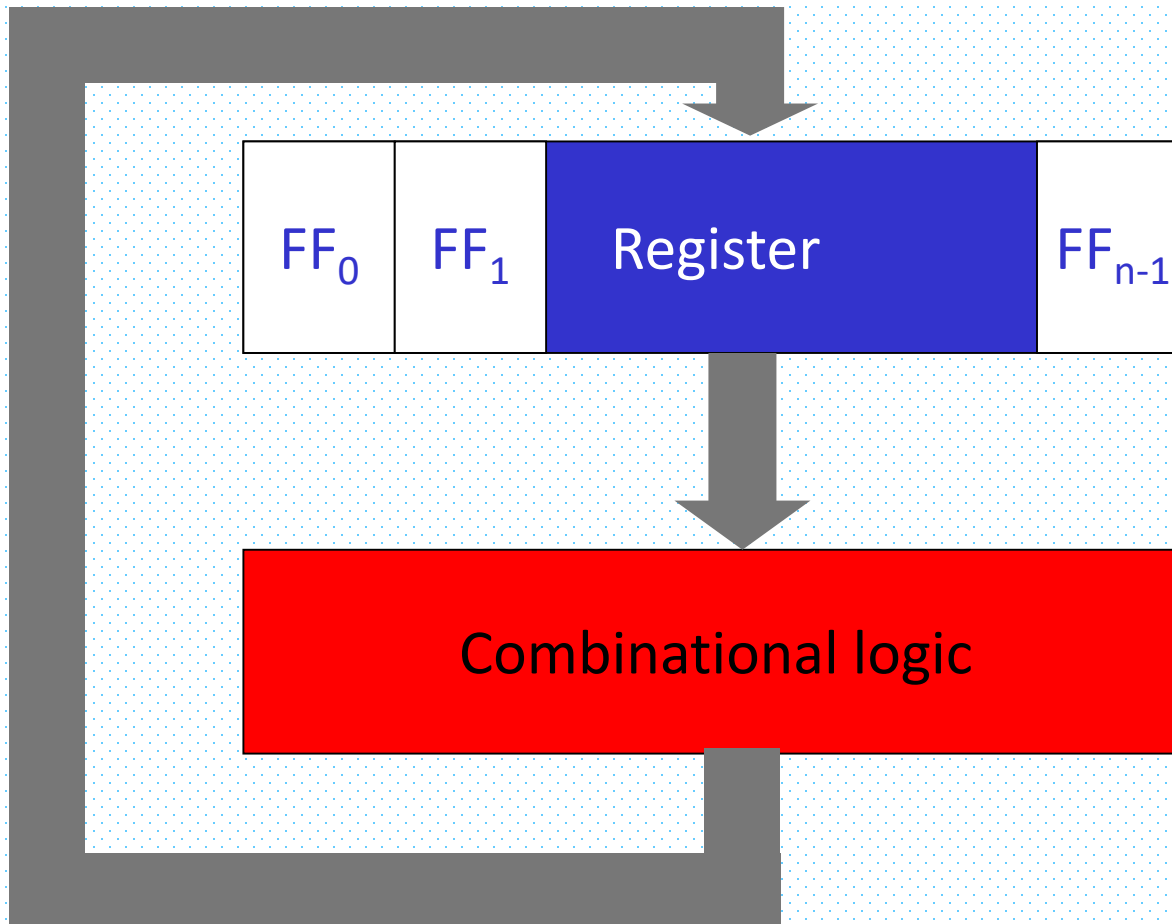
- A counter is essentially a register that goes through a predetermined sequence of states
- i.e., “Counting sequence”




Uses of Registers and Counters

- Registers are useful for storing and manipulating information
 - internal registers in microprocessors to manipulate data
- Counters are extensively used in control logic
 - PC (program counter) in microprocessors


4-bit Register

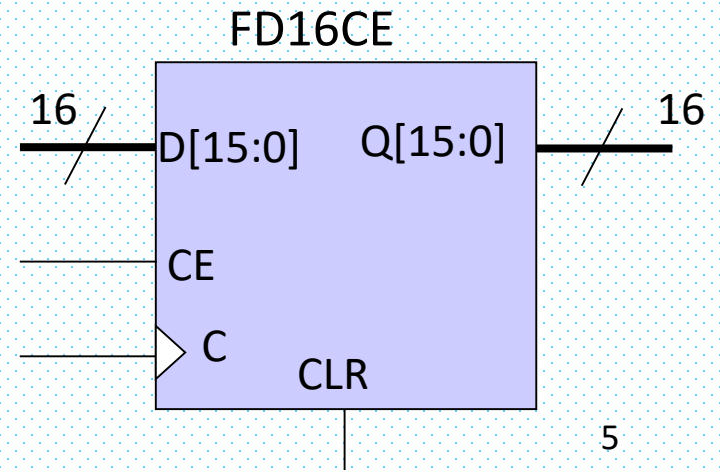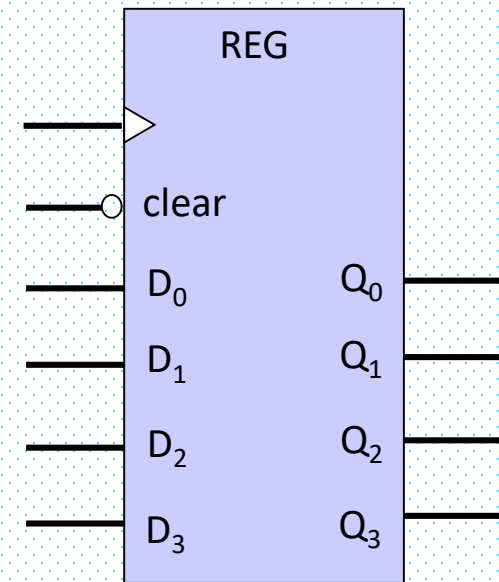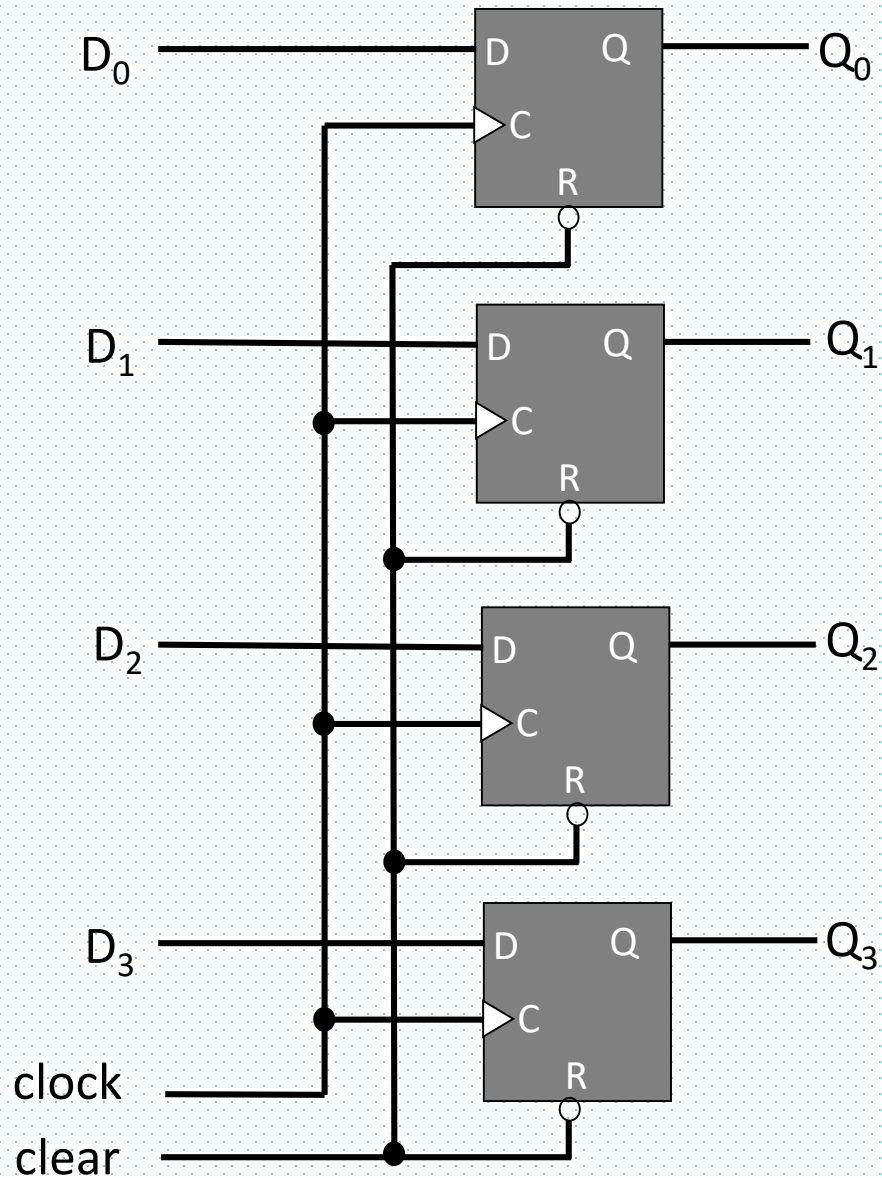


Register with Parallel Load

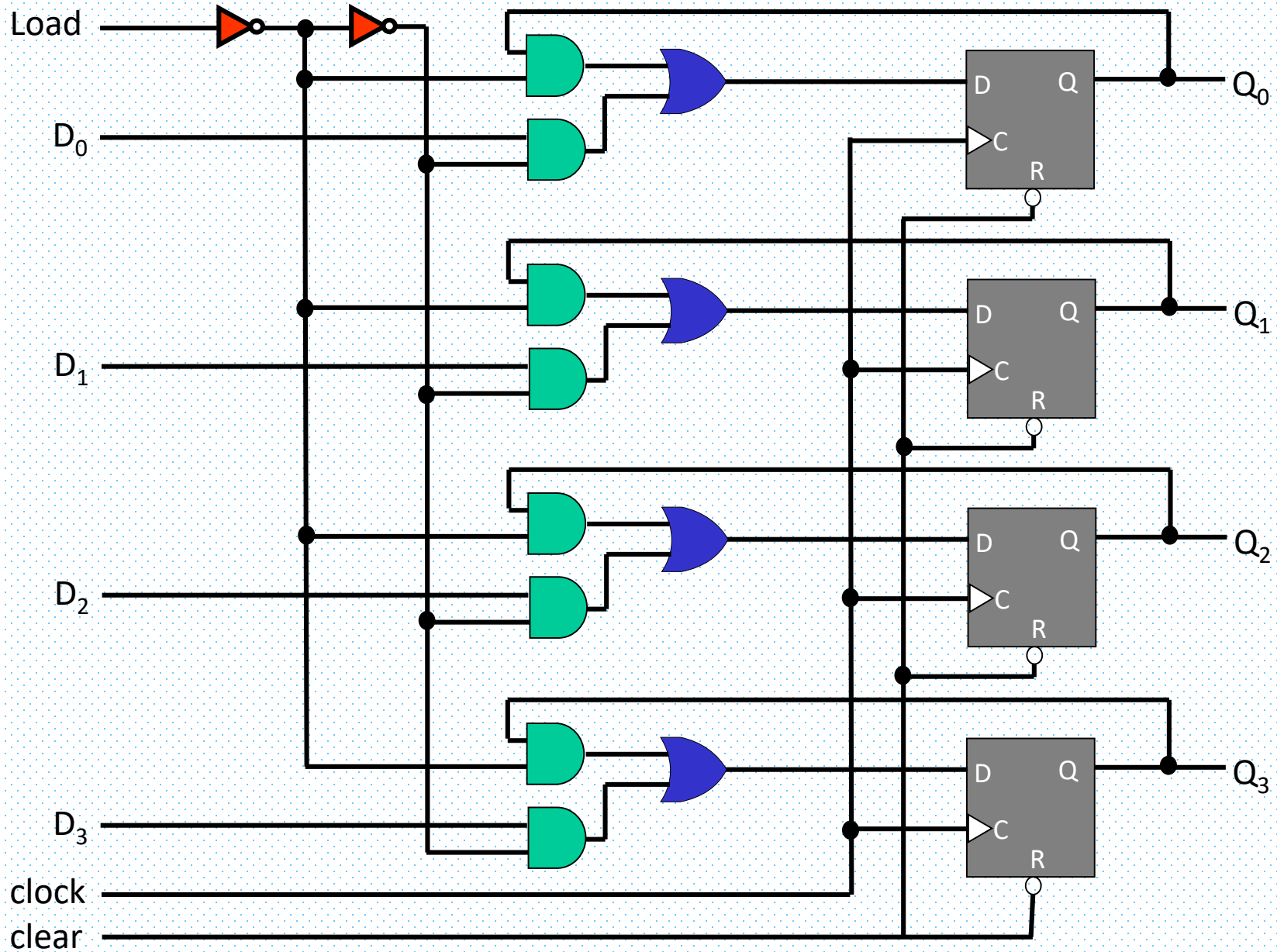

Register Transfer 1/2

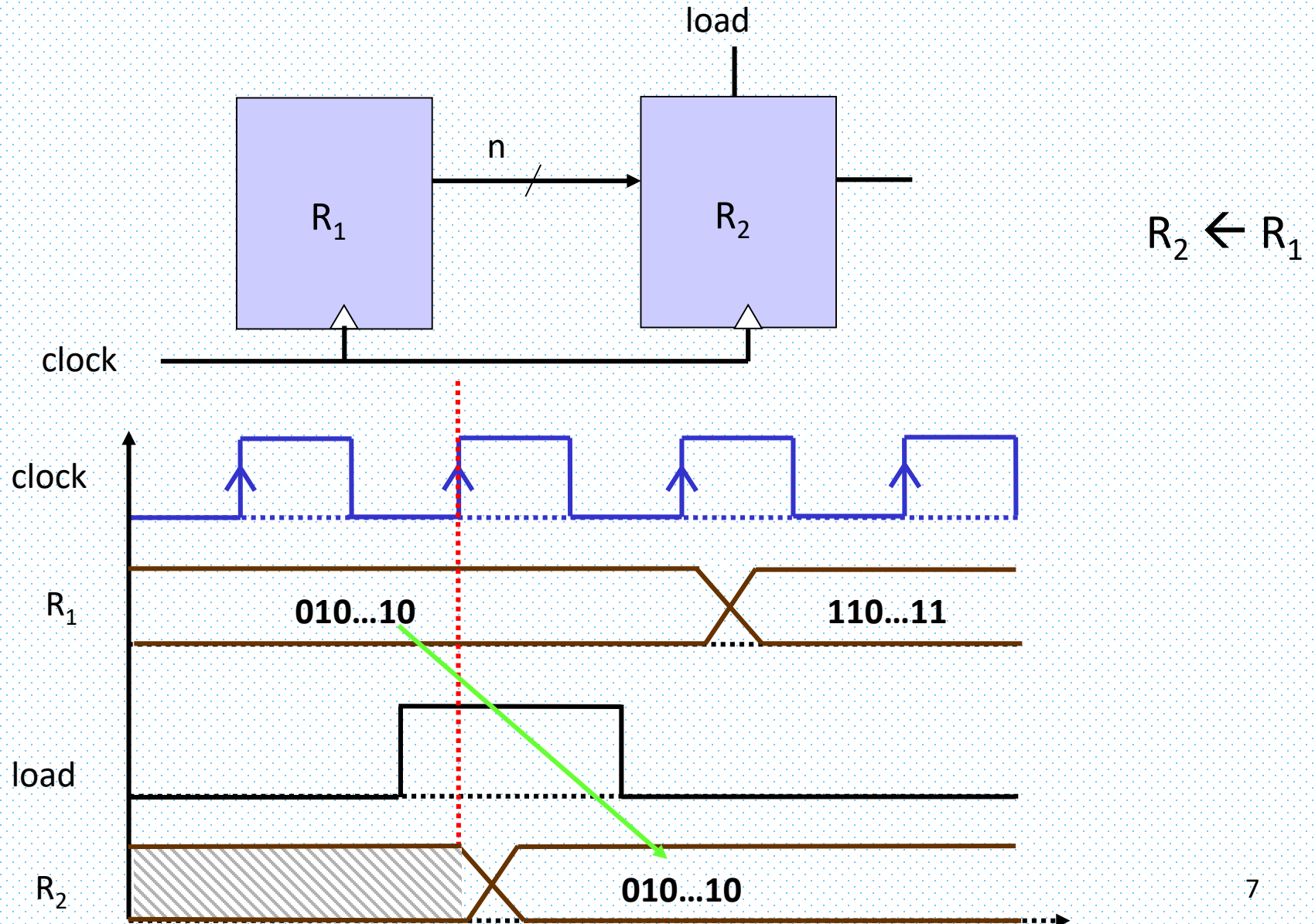


Register Transfer 2/2

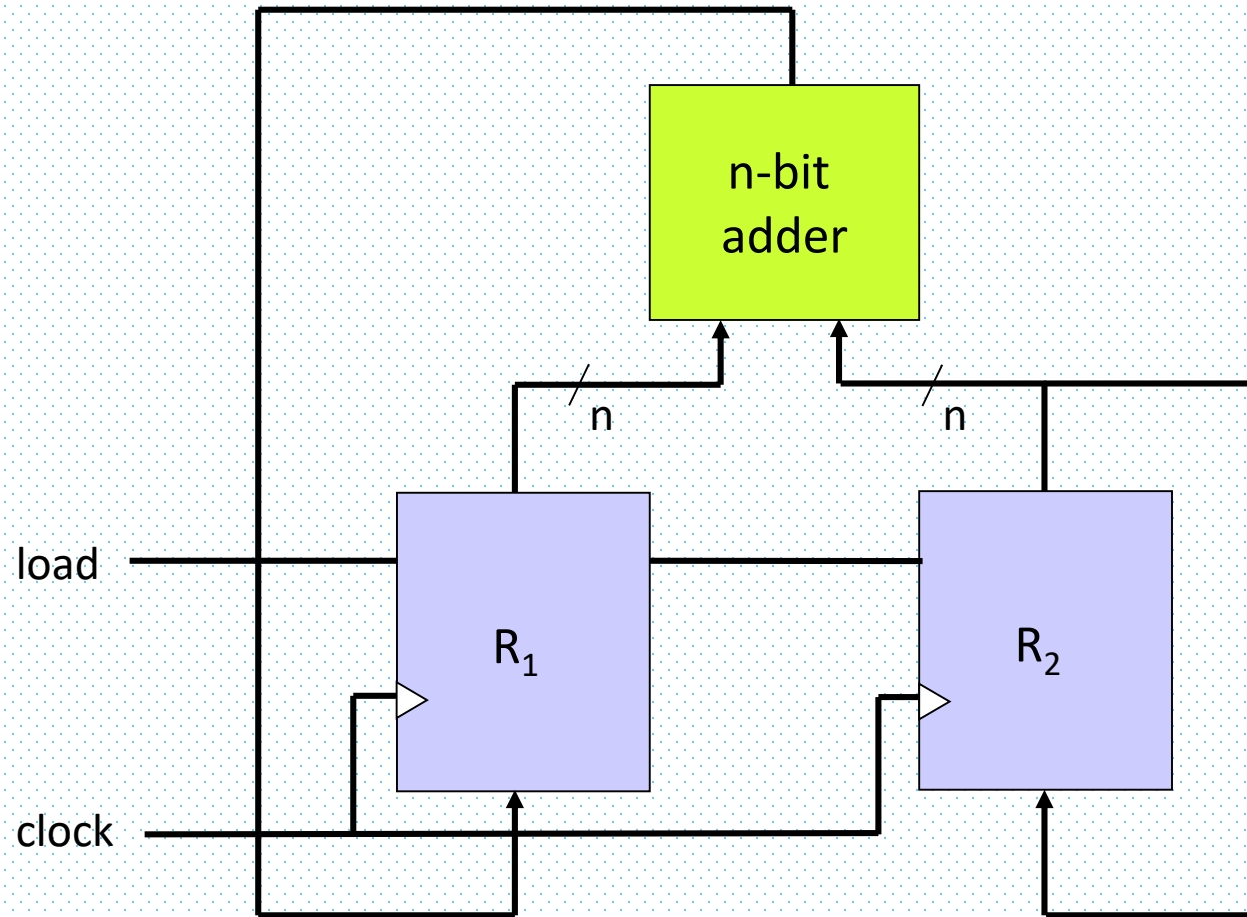

$$R_1 \leftarrow R_1 + R_2$$

Shift Registers

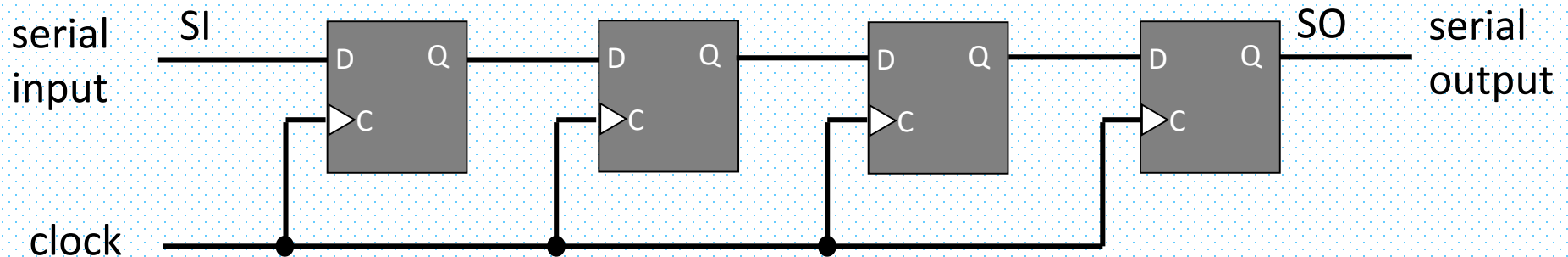
- A register capable of shifting its content in one or both directions
 - Flip-flops in cascade



- The state of an n -bit shift register can be transferred in n clock cycles

Serial Mode

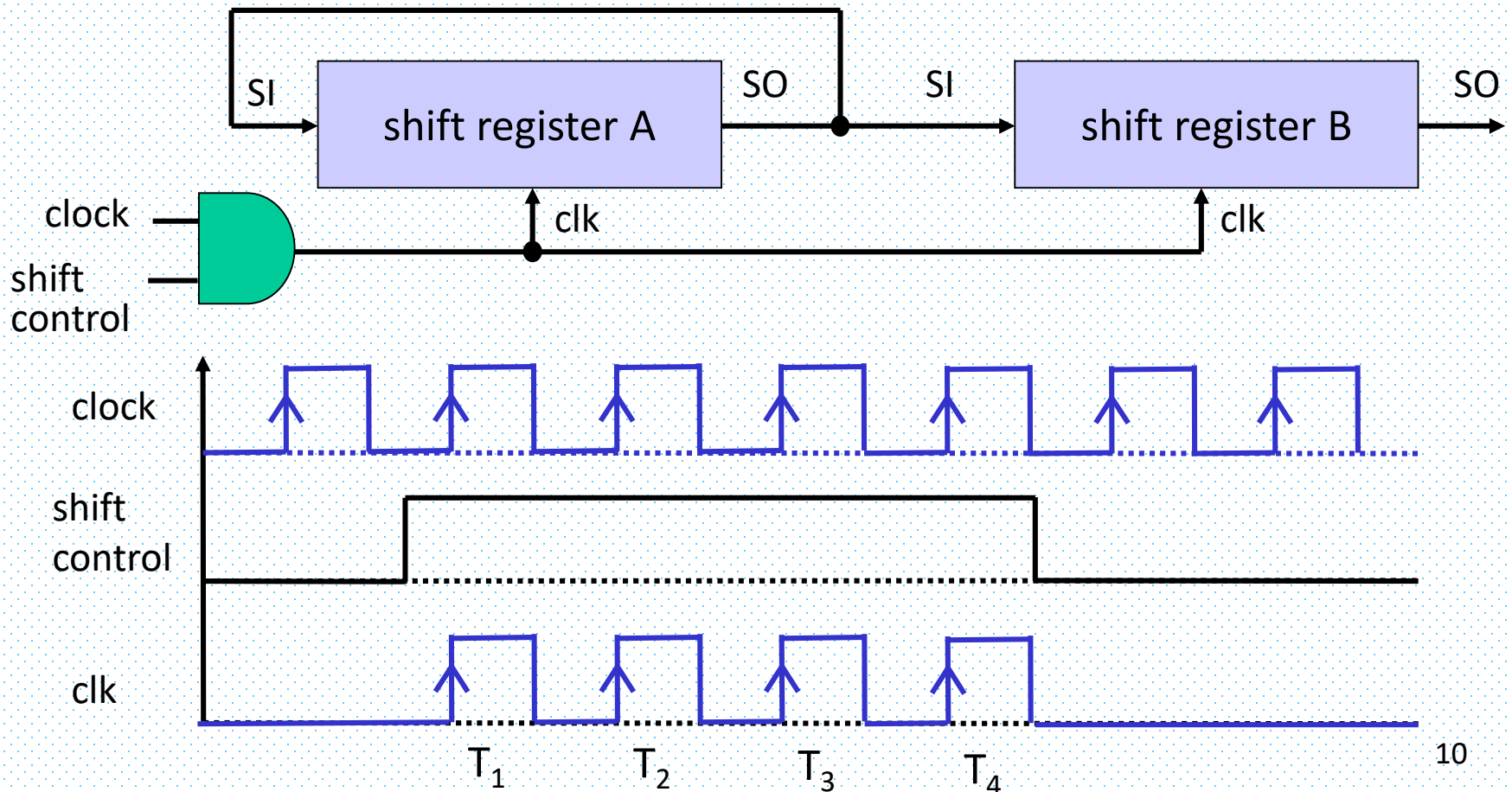- A digital system is said to operate in serial mode when information is transferred and manipulated one bit a time.





$B \leftarrow A$

Serial Transfer

- Suppose we have two 4-bit shift registers


Timing pulse	Shift register A	Shift register B
initial value	1 0 1 1	0 0 1 0
After T_1		
After T_2		
After T_3		
After T_4	1 0 1 1	1 0 1 1

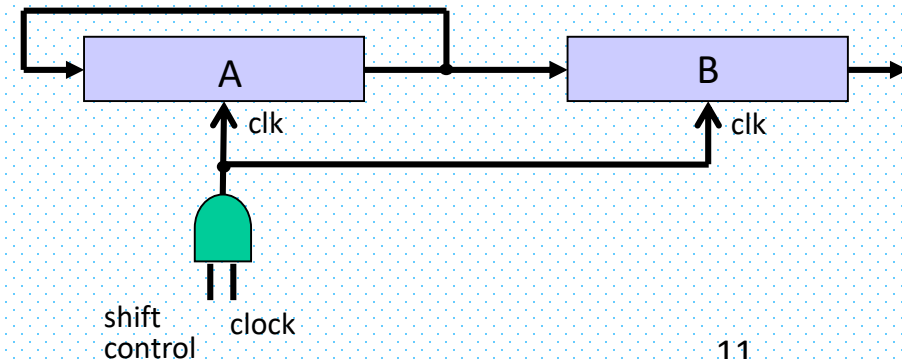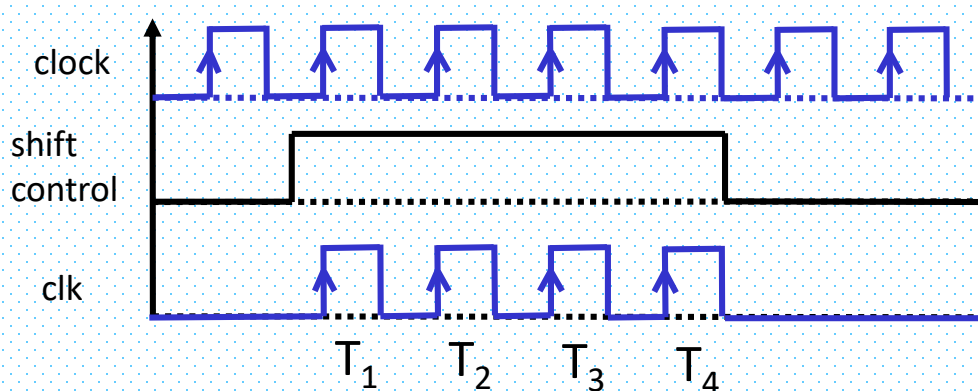

Universal Shift Register

- Capabilities:
 1. A “clear” control to set the register to 0.
 2. A “clock” input
 3. A “shift-right” control
 4. A “shift-left” control
 5. n input lines & a “parallel-load” control
 6. n parallel output lines

4-Bit Universal Shift Register

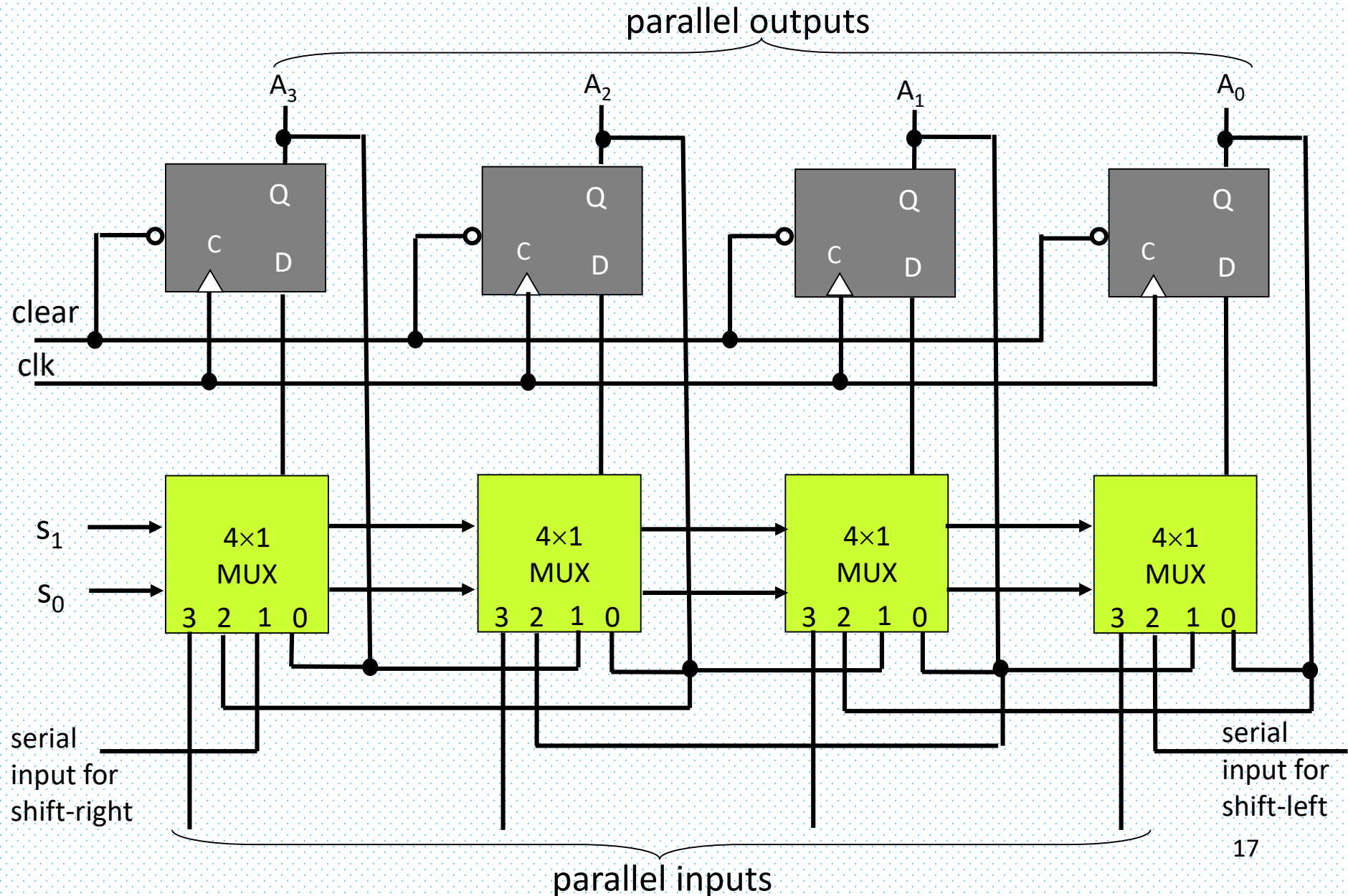

Universal Shift Register

Mode Control		
s_1	s_0	Register operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

Coding Universal 32-bit Shift Register

```
module SR_32_BEH(
    output reg [31:0]  A_par,           // Register output
    input      [31:0]  I_par,           // Parallel input
    input      s1, s0,                 // selection inputs
                                   MSB_in, LSB_in, // Serial inputs
                                   clk, clear);    // clock, reset

    always @(posedge clk, negedge clear)
        if(~clear) A_par <= 32'h00000000;
        else
            case ({s1,s0})
                2b'00: A_par <= A_par           // no change
                2b'01: A_par <= {MSB_in, A_par[31:1]}; // shift right
                2b'10: A_par <= {A_par[30:0], LSB_in}; // shift right
                2b'11: A_par <= I_par;           // parallel load
            endcase
endmodule
```

Counters

- registers that go through a prescribed sequence of states upon the application of input pulses
 - input pulses are usually clock pulses
- Example: n-bit binary counter
 - count in binary from 0 to 2^n-1
- Classification
 1. Synchronous counters
 - flip-flops receive the same common clock as *the* pulse
 2. Ripple counters
 - flip-flop output transition serves as *the* pulse to trigger other flip-flops


Binary Ripple Counter

3-bit binary ripple counter


0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0

- Idea:
 - to connect the output of one flip-flop to the C input of the next high-order flip-flop
- We need “complementing” flip-flops
 - We can use T flip-flops to obtain complementing flip-flops or
 - JK flip-flops with its inputs are tied together or
 - D flip-flops with the **complement** output connected to the D input.


4-bit Binary Ripple Counter

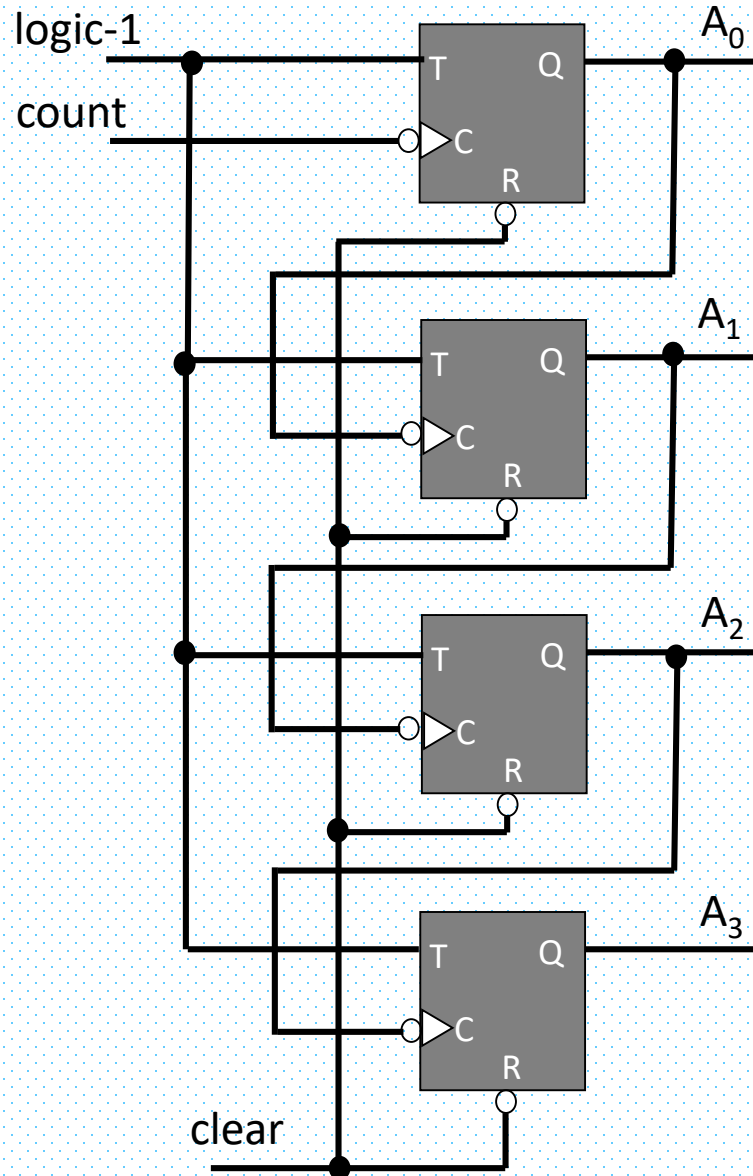

0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
0	0	0	0	0

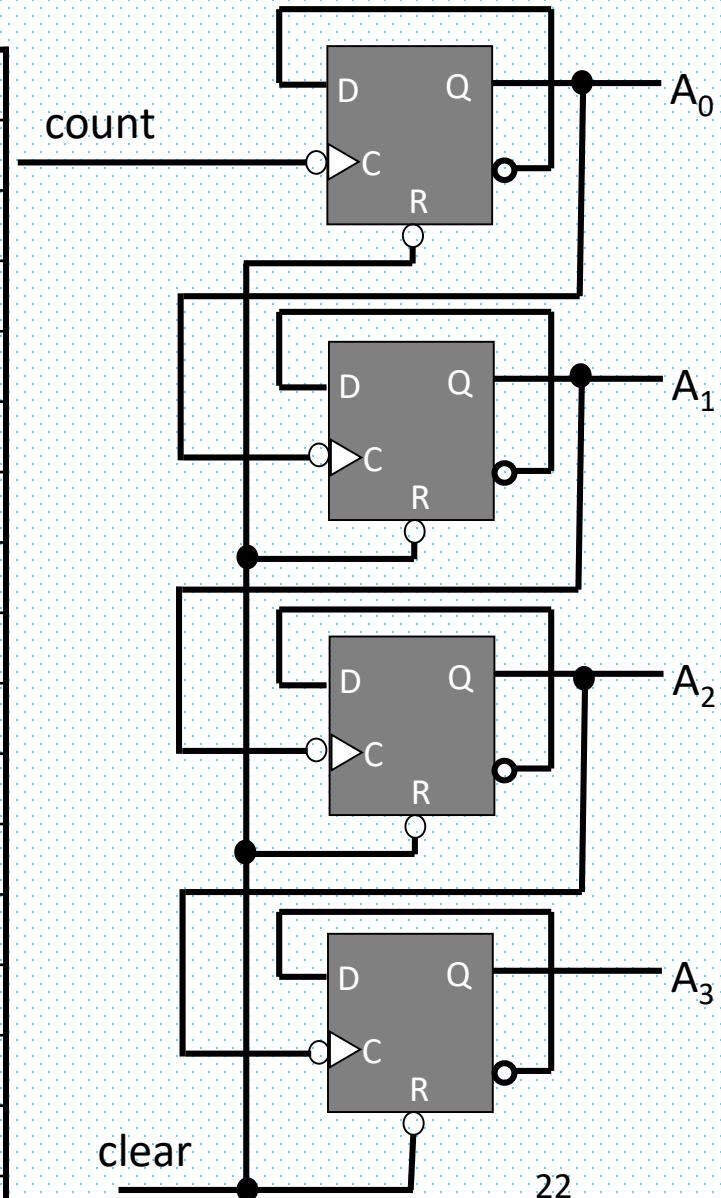

4-bit Binary Ripple Counter

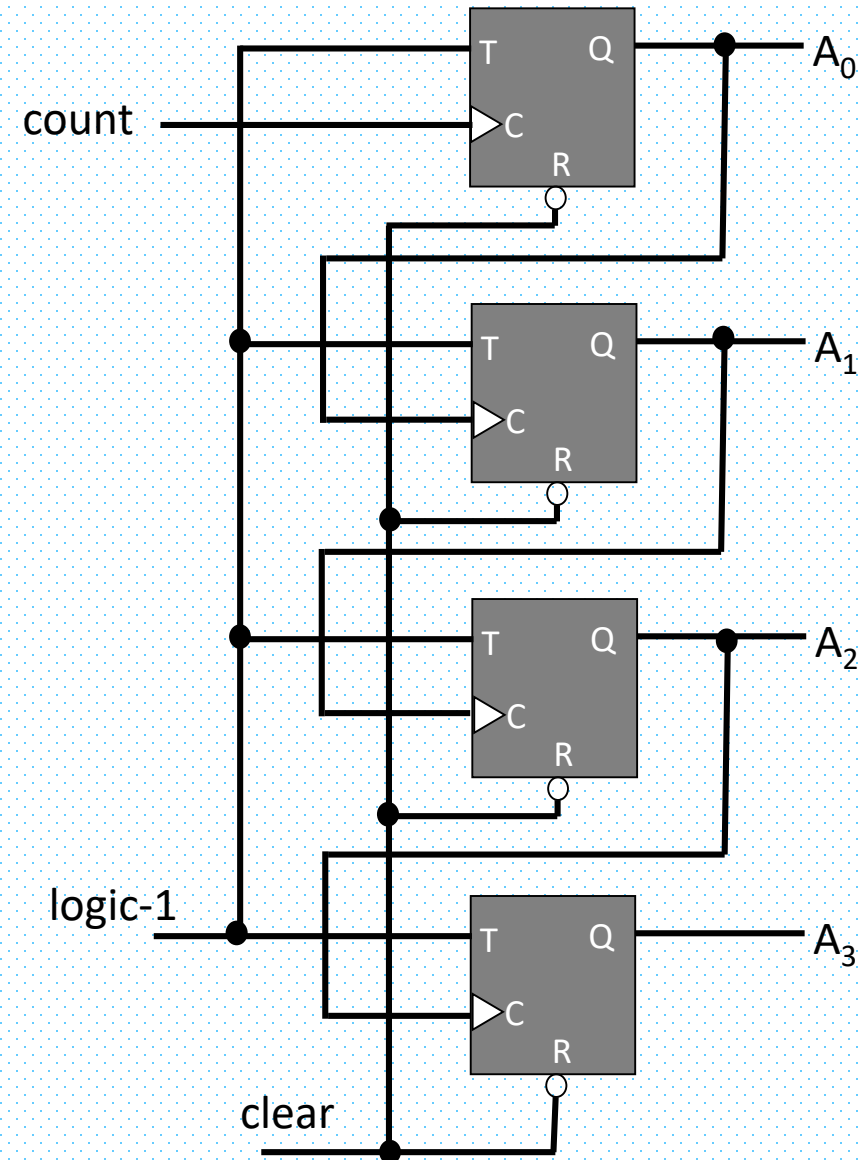


- Suppose the current state is **1100**
- What is the next state?

Verilog of Binary Ripple Counter

```
`timescale 1ns / 1ps  
module TFF(Q, T, clk, reset);  
    input T,reset,clk;  
    output reg Q;  
    always @(negedge reset, negedge clk)  
        if(reset) Q <= 1'b0;  
        else Q <= #1 T^Q;  
endmodule  
module RippleCounter(  
    output [3:0] A,  
    input Count, reset);  
    TFF FF0(A[0], 1'b1, Count, reset);  
    TFF FF1(A[1], 1'b1, A[0], reset);  
    TFF FF2(A[2], 1'b1, A[1], reset);  
    TFF FF3(A[3], 1'b1, A[2], reset);  
endmodule
```

```
module TestRippleCounter;  
    reg Cnt;  
    reg Rst;  
    wire [3:0] A;  
    // Instantiate ripple counter  
    RippleCounter Counter(A, Cnt, Rst);  
    always  
        #5 Cnt = ~Cnt;  
    initial  
        begin  
            Cnt = 1'b0;  
            Rst = 1'b0;  
            #4 Rst = 1'b1;  
        end  
    initial #170 $finish;  
endmodule
```

Simulation

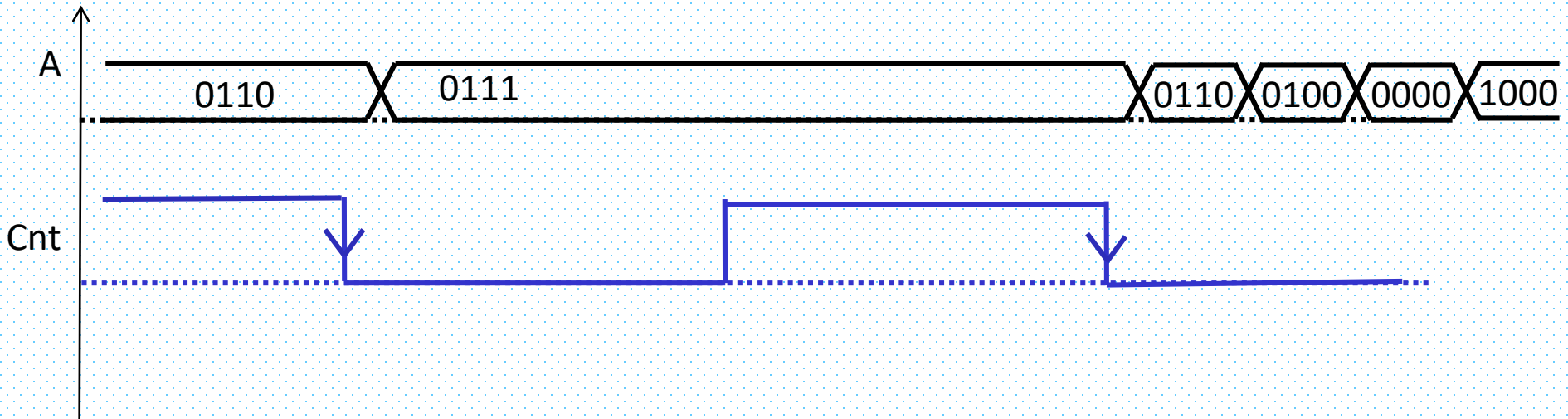


Synchronous Counters


- There is a common clock
 - that triggers all flip-flops simultaneously
 - If $T = 0$ or $J = K = 0$ the flip-flop does not change state.
 - If $T = 1$ or $J = K = 1$ the flip-flop does change state.
- Design procedure is so simple
 - no need for going through sequential logic design process
 - A_0 is always complemented
 - A_1 is complemented when $A_0 = 1$
 - A_2 is complemented when $A_0 = 1$ and $A_1 = 1$
 - so on

0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0


4-bit Binary Synchronous Counter

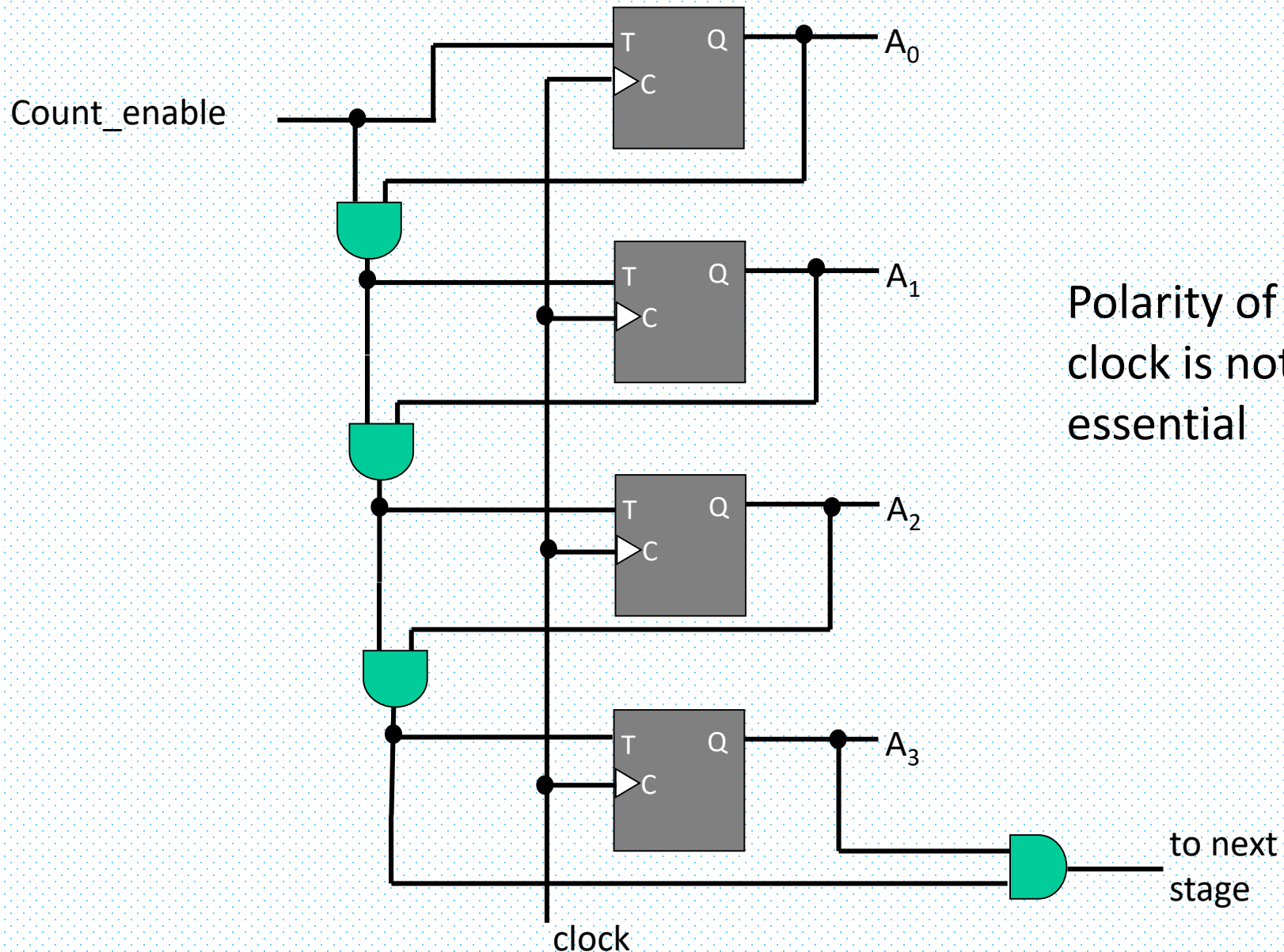

Timing of Synchronous Counters

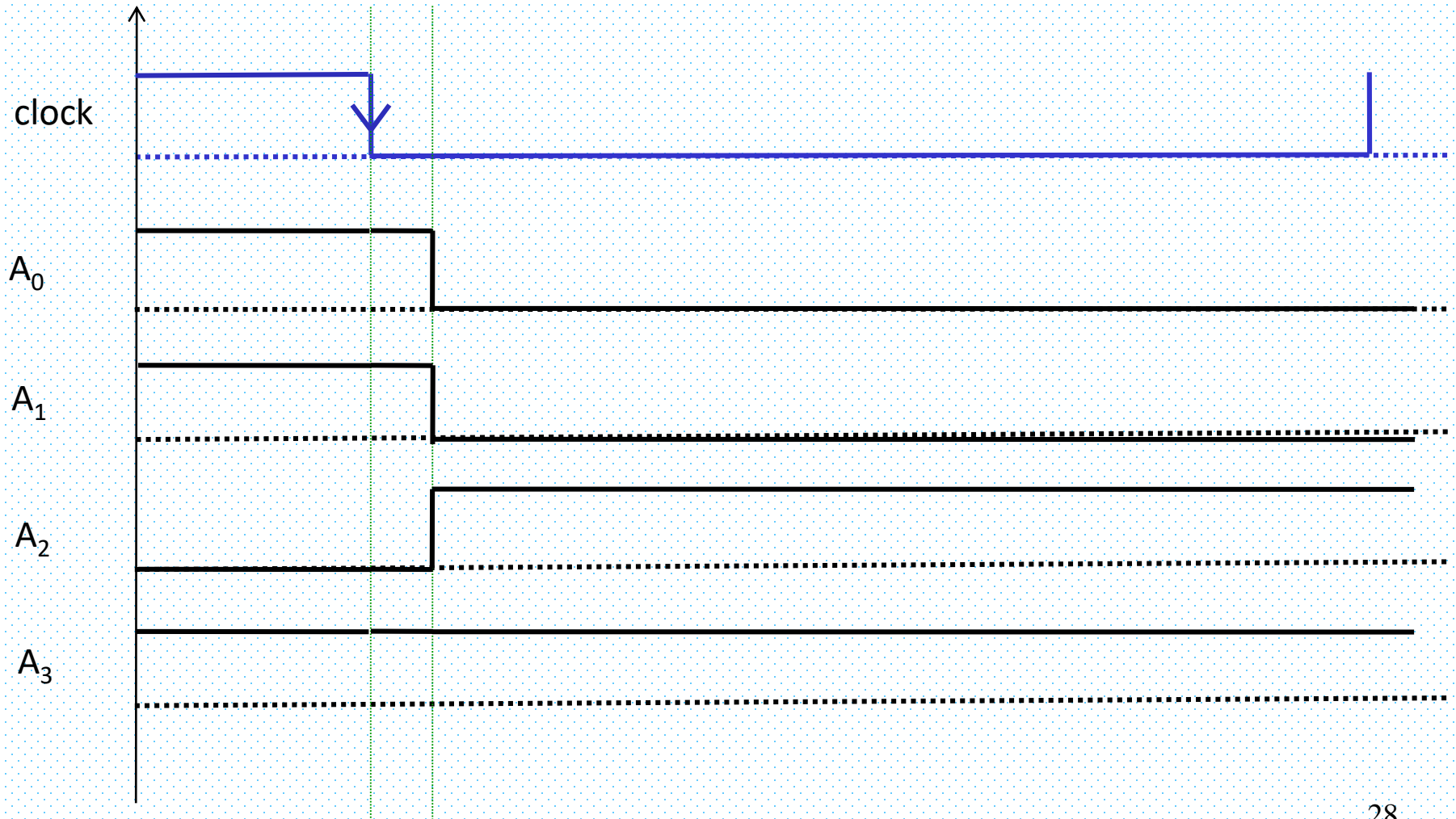

Timing of Ripple Counters

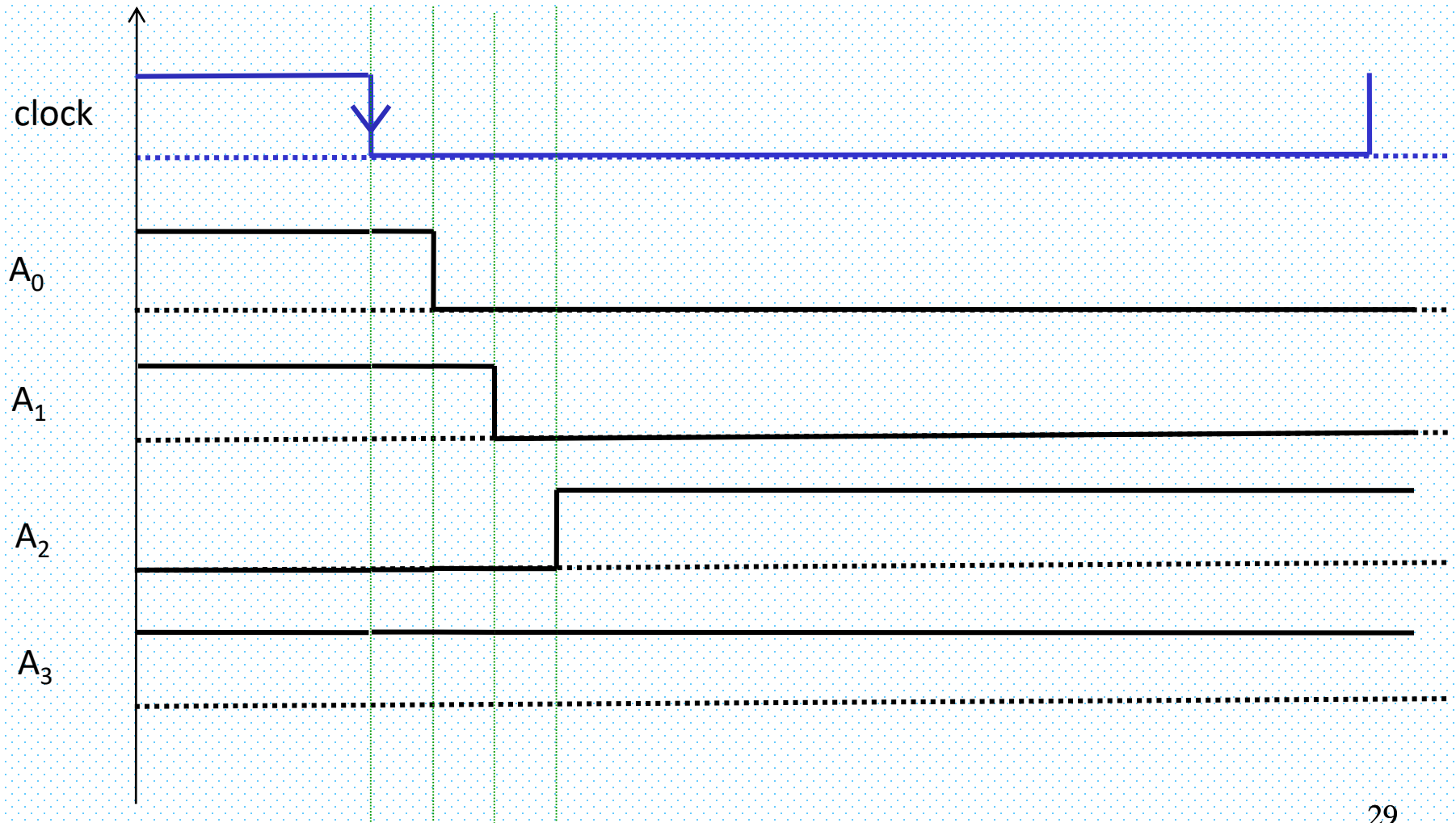


Up-Down Binary Counter

- When counting downward
 - the least significant bit is always complemented (with each clock pulse)
 - A bit in any other position is complemented if all lower significant bits are equal to 0.
 - For example: 0 1 0 0
 - Next state:
 - For example: 1 1 0 0
 - Next state:


0	0 0 0
7	1 1 1
6	1 1 0
5	1 0 1
4	1 0 0
3	0 1 1
2	0 1 0
1	0 0 1
0	0 0 0

Up-Down Binary Counter

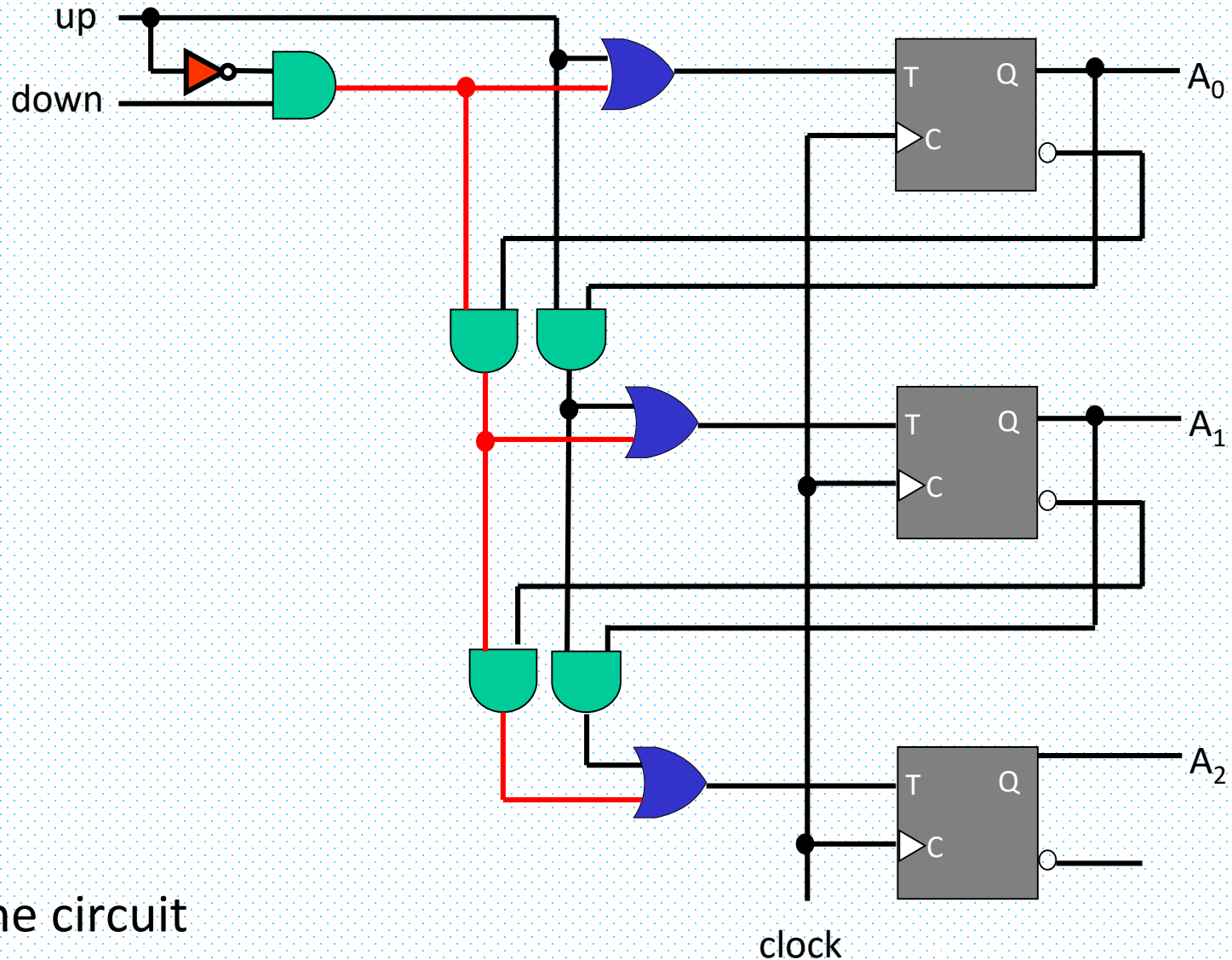

- The circuit

Binary Counter with Parallel Load

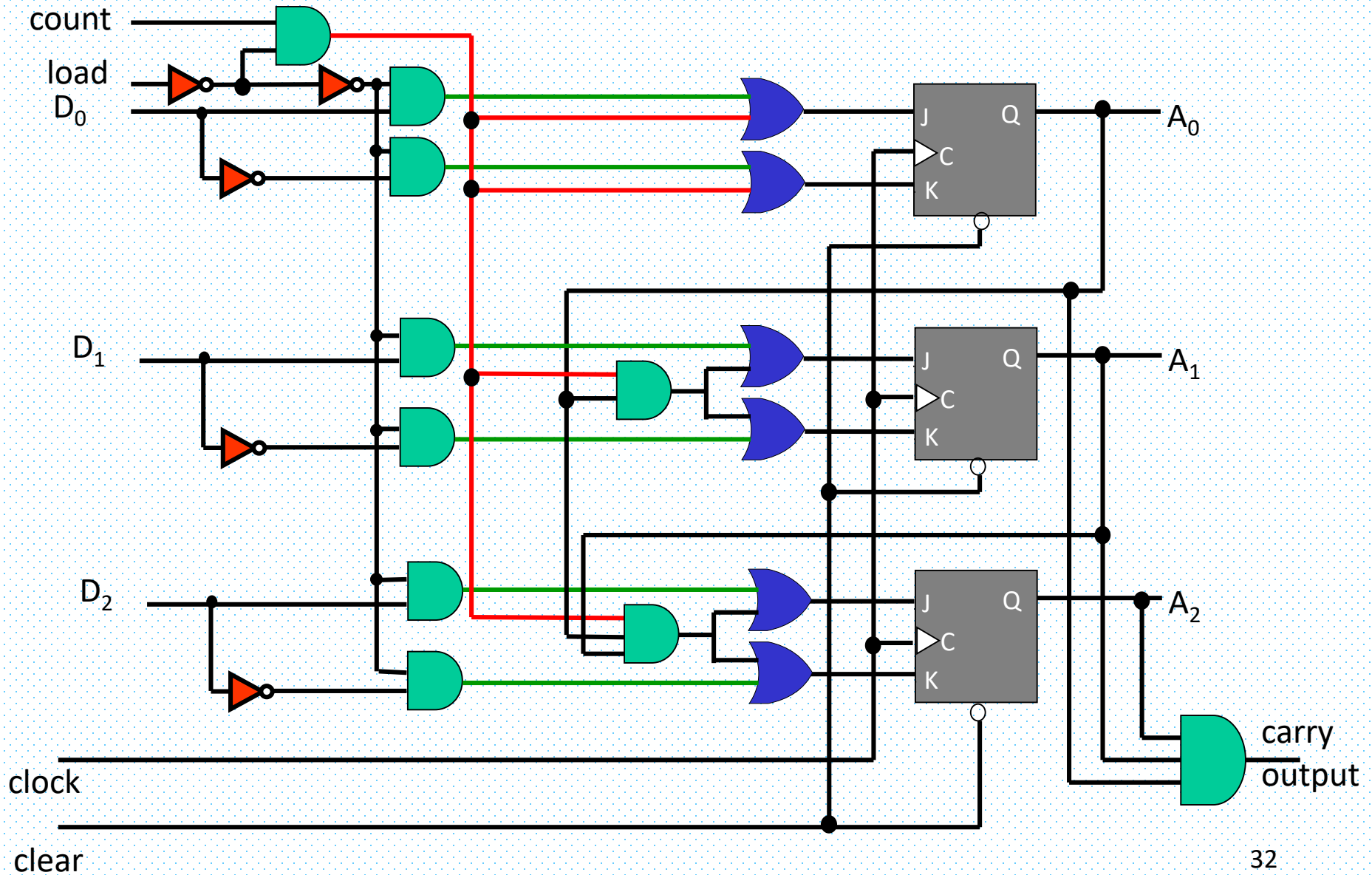

Binary Counter with Parallel Load

Function Table

clear	clock	load	Count	Function
0	X	X	X	clear to 0
1	↑	1	X	load inputs
1	↑	0	1	count up
1	↑	0	0	no change


Verilog of Binary Counter

```
module BinaryCounter_8_BEH(  
    output reg [7:0]      A_cnt,           // Counter output  
    output               C_out,          // If a cycle is completed  
    input      [7:0]      Data_in,       // Parallel input  
    input               Count,           // Active high to count  
                                Load,     // Active high to load  
                                clk, clear); // clock, reset  
  
    assign C_out = Count & (~Load) & (A_cnt == 8'hFF);  
    always @(posedge clk, negedge clear)  
        if(~clear) A_cnt <= 8'h00;  
        else if(Load) A_cnt <= Data_in;  
        else if(Count) A_cnt <= A_cnt + 1'b1;  
        else A_cnt <= A_cnt;  
  
endmodule
```

Other Counters

- Ring Counter

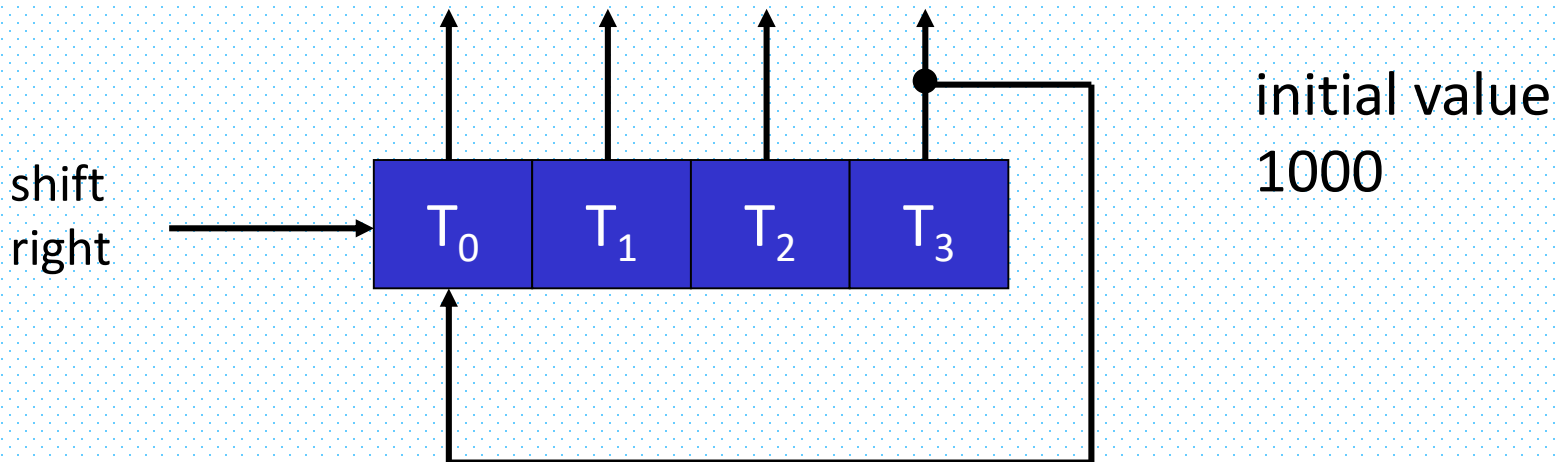- A ring counter is a circular shift register with only one flip-flop being set at any particular time, all others are cleared.




- Usage

- Timing signals control the sequence of operations in a digital system


Ring Counter

- Sequence of timing signals

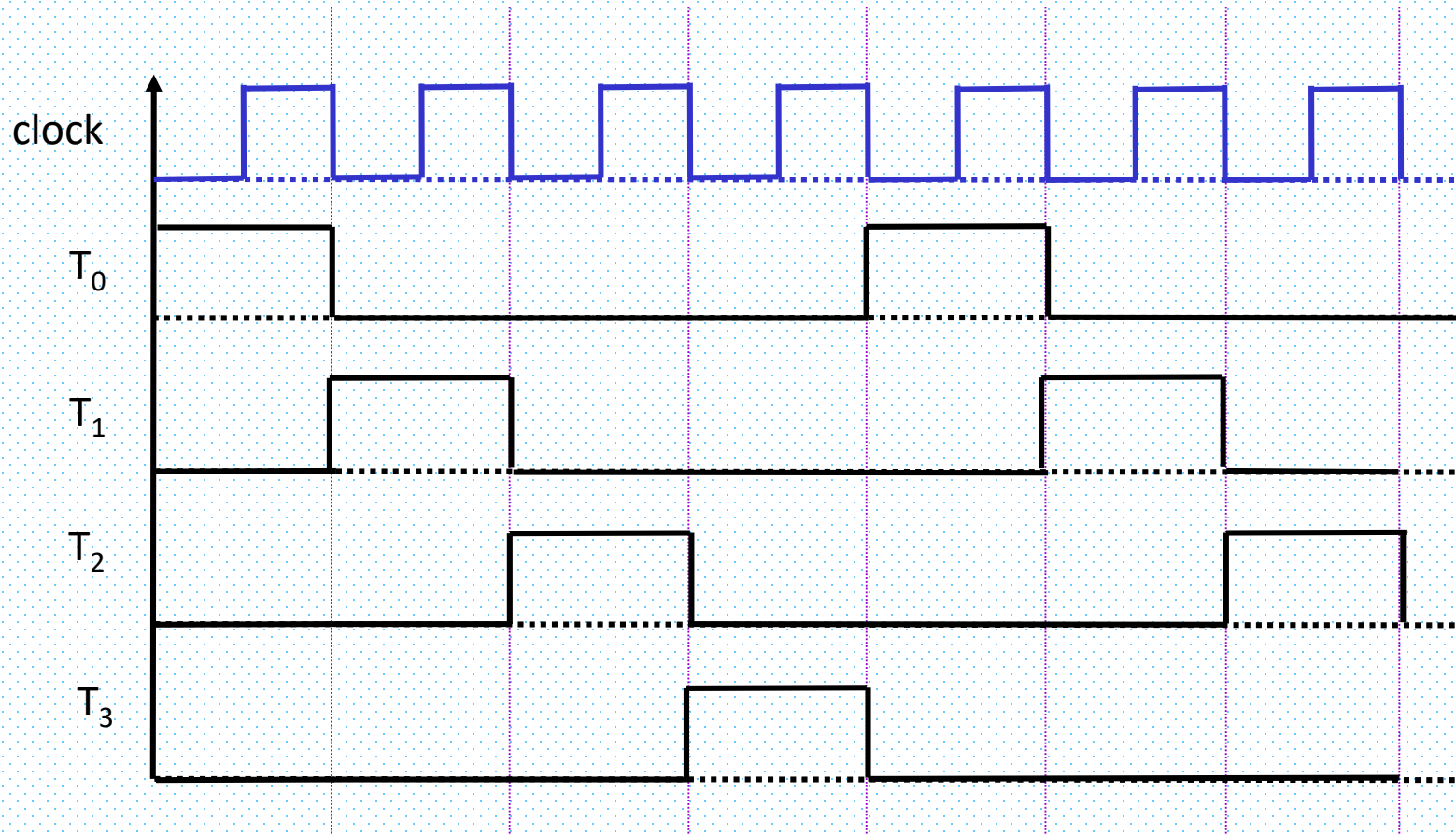

Ring Counter

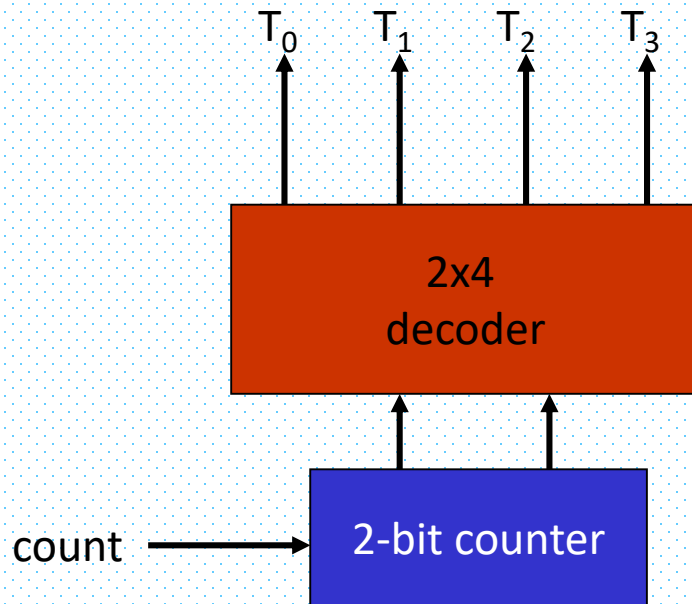- To generate 2^n timing signals,
 - we need a shift register with 2^n flip-flops
- or, we can construct the ring counter with a binary counter and a decoder



Cost:


- 2 flip-flops
- 2-to-4 line decoder

Cost in general case:

- n flip-flops
- n -to- 2^n line decoder
 - 2^n n -input AND gates
 - n NOT gates

Johnson Counter

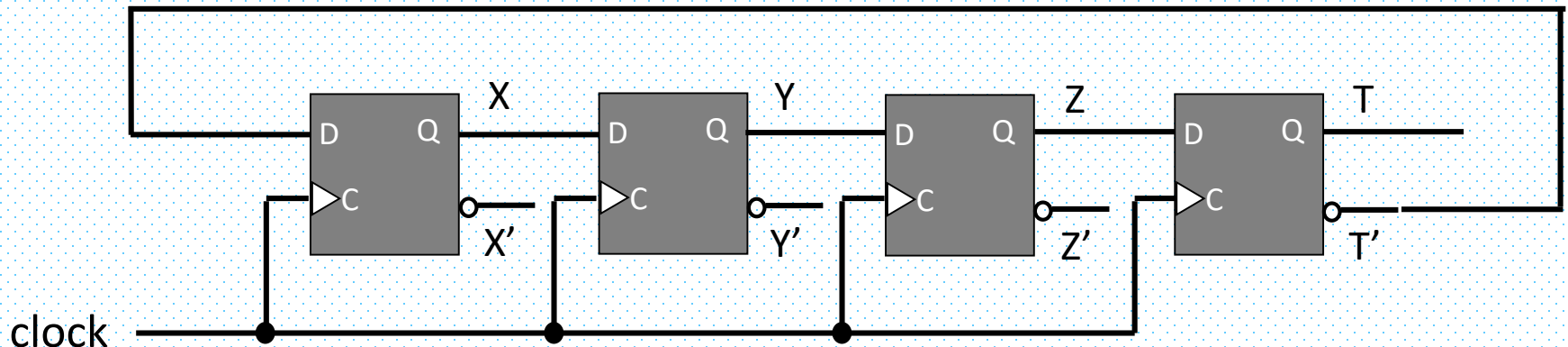- A k-bit ring counter can generate k distinguishable states
- The number of states can be doubled if the shift register is connected as a switch-tail ring counter




Johnson Counter

- Count sequence and required decoding

sequence number	Flip-flop outputs				Output
	X	Y	Z	T	
1	0	0	0	0	$S_0 = X'T'$
2					$S_1 = XY'$
3					$S_2 = YZ'$
4					$S_3 = ZT'$
5					$S_4 = XT$
6					$S_5 = X'Y$
7					$S_6 = Y'Z$
8					$S_7 = Z'T$



Johnson Counter

- Decoding circuit

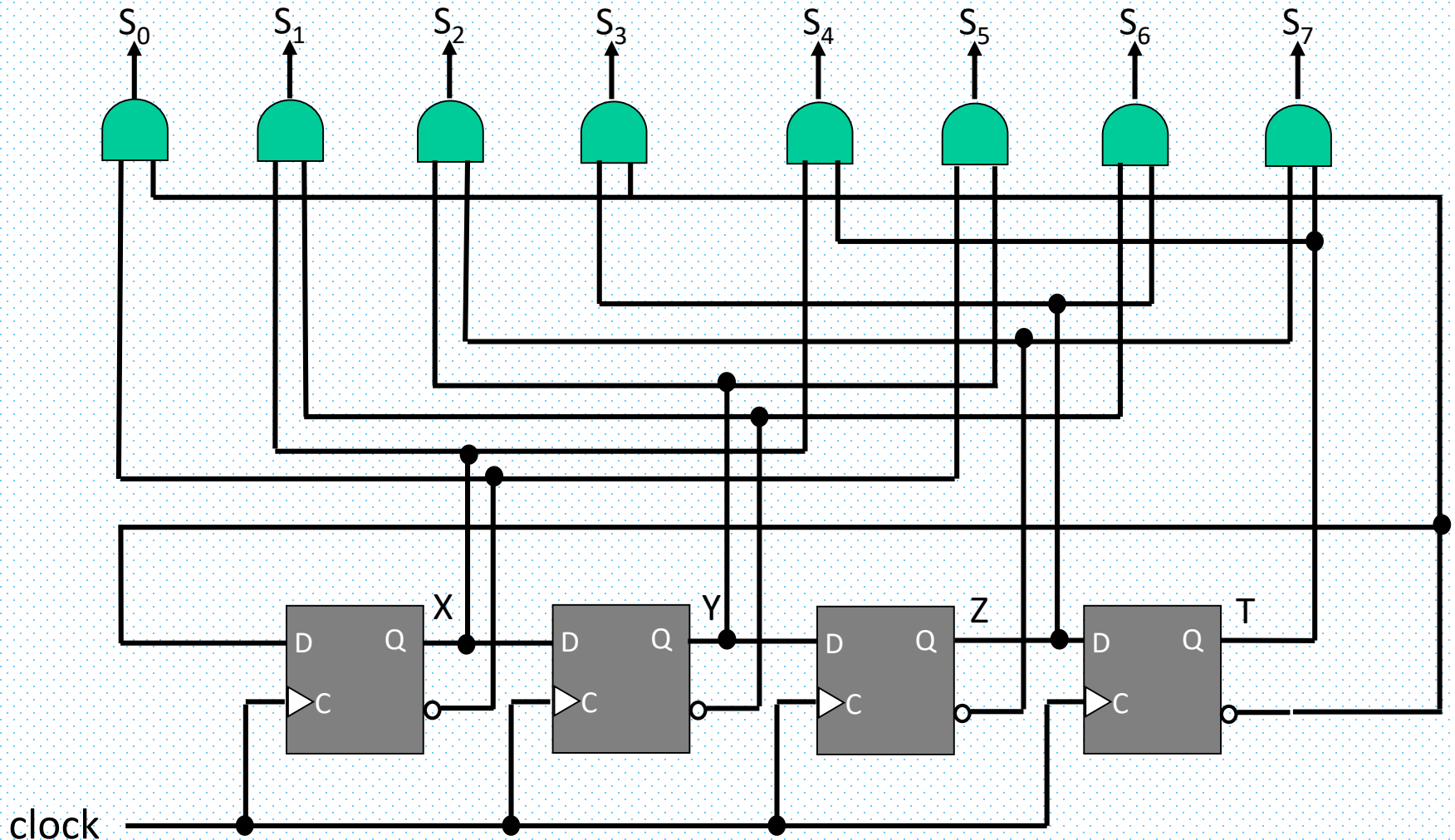


Unused States in Counters

- 4-bit Johnson counter

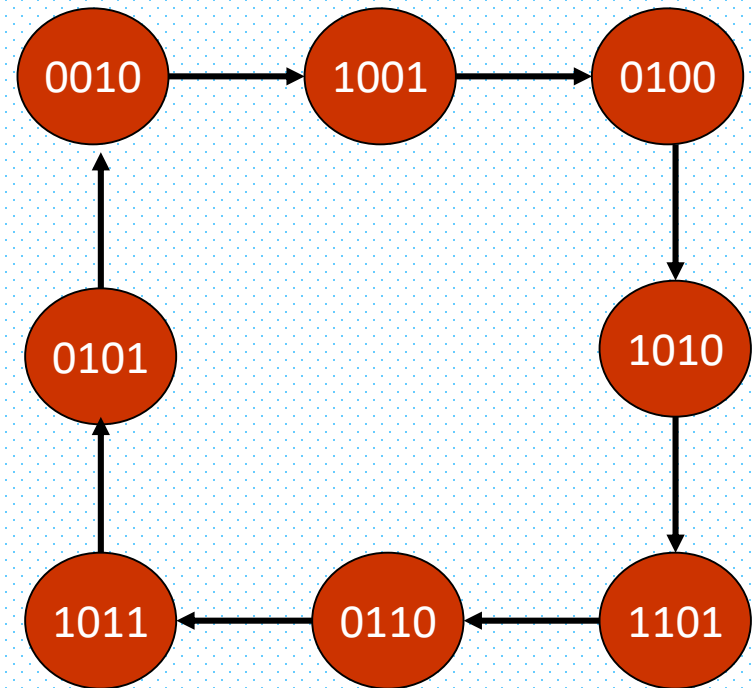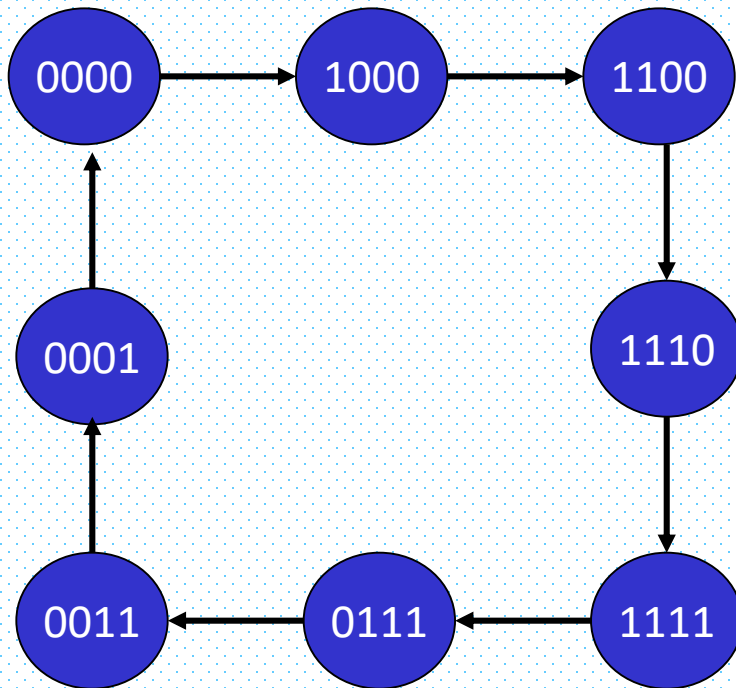

Correction

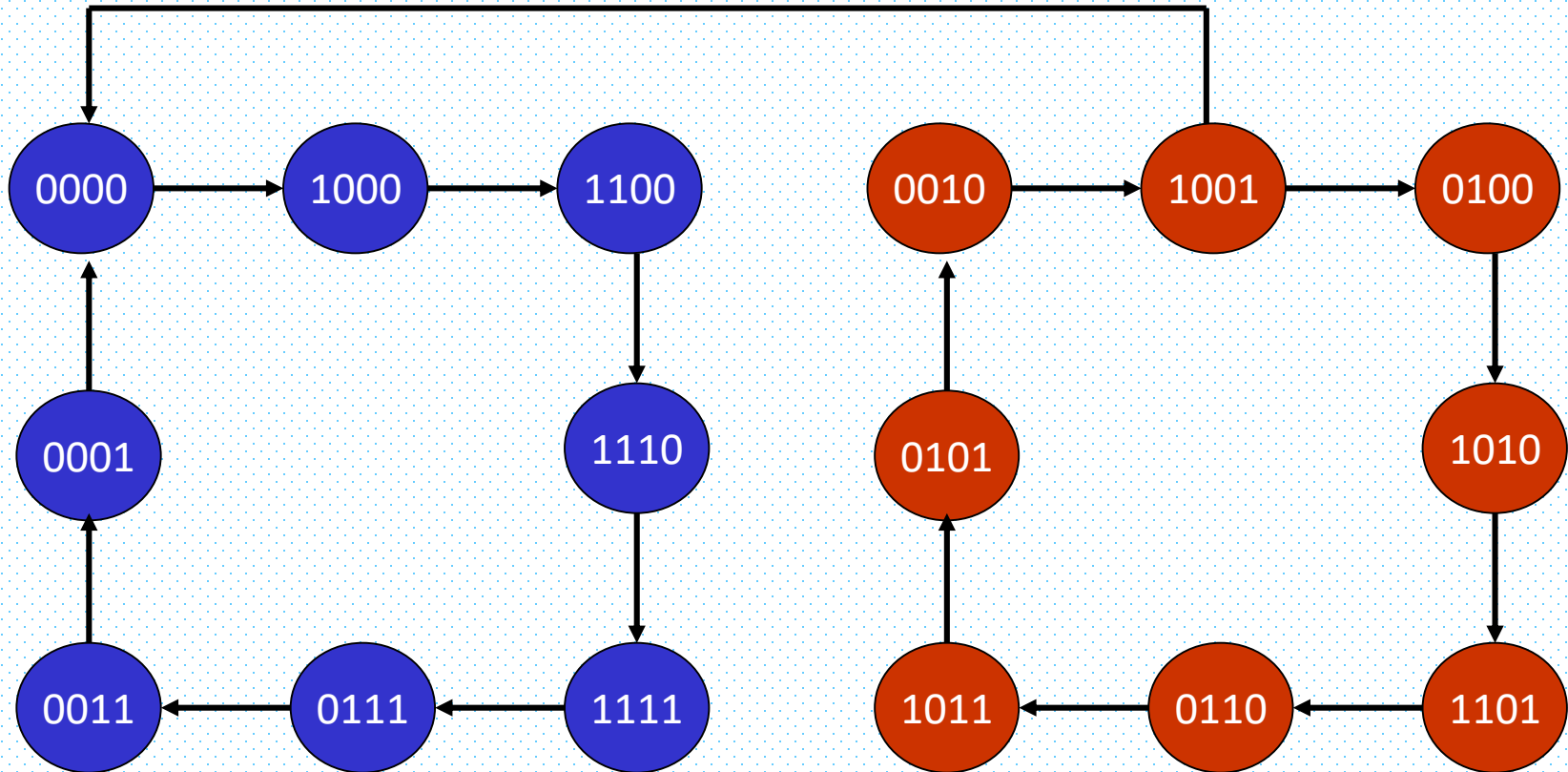

Johnson Counter

Present State				Next State			
X	Y	Z	T	X	Y	Z	T
0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0
1	1	0	0	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	1
1	0	0	1	0	0	0	0
0	1	0	0	1	0	1	0
1	0	1	0	1	1	0	1
1	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	0	0	1	0

K-Maps

		ZT			
		00	01	11	10
XY	00	1			1
	01	1			1
	11	1			1
	10	1			1

$$X(t+1) = T'$$

		ZT			
		00	01	11	10
XY	00				
	01				
	11	1	1	1	1
	10	1	0	1	1

$$Y(t+1) = XY + XZ + XT'$$

		ZT			
		00	01	11	10
XY	00				
	01	1	1	1	1
	11	1	1	1	1
	10				

$$Z(t+1) = Y$$

		ZT			
		00	01	11	10
XY	00			1	1
	01			1	1
	11			1	1
	10			1	1

$$T(t+1) = Z$$

Unused States in Counters

- Remedy $X(t+1) = T'$ $Y(t+1) = XY + XZ + XT'$
 $Z(t+1) = Y$ $T(t+1) = Z$

